```
Case 4
 path A-wa- U4- w5- U2-w8-U5-w6
      input delay = 0
     AND (U4)
       input fransition = 0.9
     Cell delay = 0.3553
        Cell transition: 0-3854
    FF (U2)
       setup time = 0.2802
      hold time = 0.0417
      tca = 0.5275
      output transition = 0.5081
     A-wa-U3-w4-U1-w2-U4-w5-U2-w8-U5
path
   input delay = 0
     INV (N3)
        input transition = 0.9
        cell delay = 0.3598
        cell transition = 0.3987
    FF (U1)
        setup time = 0.2411
         hold time = 0.0560
         tia = 0.5006
         output transition = 0-38294
   AND (U4)
       Input transition = 0.38294
       cell delay = 0.3857
       cell transition = 0.3327
   FF (U2)
       setup time = 0.2804
       hold time : 0.0417
       tig = 0-5279
```

Timing analysis (Path 1)

Input to Reg

arrival time = 0 + 0.3553 = 0.3598required time = 3 + 1 - 0.2802 = 3.7198slack = 3.36

Timing analysis (Path 2)

Input to Reg

arrival time = 0,3598

required time = 3+4-0,2411 = 3.7589

Slack = 3-3991

Reg to Reg

arrival fime = 1 + 0.5006 + 0.3857 = 1.8863required time = 3 + 1 - 0.2804 = 3.7196slack = 1.8333